



**United International University (UIU)**  
**Department of Computer Science and Engineering**  
**CSE 1325: DIGITAL LOGIC DESIGN, Final Summer 2024**

Total Marks: **50**, Duration: 2 hours

Answer ALL Questions


**Any examinee found adopting unfair means will be expelled from the trimester /  
program as per UIU disciplinary rules**

1. You have created a new flip-flop X which has the following excitation table:

Q(t)	Q(t+1)	X
0	0	1
0	1	0
1	0	1
1	1	0

Design a clocked sequential circuit that recognizes the 4-bit input sequence 0000, including overlap of one bit using X Flip-Flops. For such a circuit, complete the following steps:

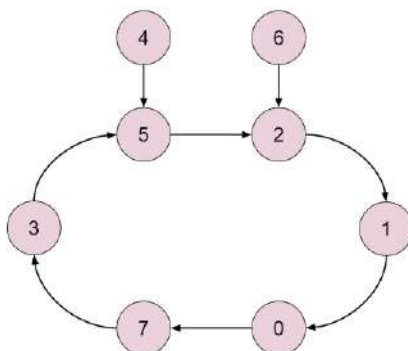- A. Draw the state diagram while assigning the states as gray code. [2]
  - B. What changes would be made in the state diagram if the sequence was non-overlapping. (You can draw only the modified part) [1]
  - C. Draw the state table with output and input function for X flip-flop (considering overlapping sequence). [3]
  - D. Minimize the functions of output and flip-flop inputs. [2]
  - E. Suppose an input bit stream "00000000" is given. Write down the output stream considering: [2]
    - i. Overlapping sequence
    - ii. Non-overlapping sequence
2. You want to design an arbitrary synchronous counter circuit using D flip-flops that counts according to the sequence given in the figure.



- A. Draw the state table with flip-flop inputs. [4]
- B. Show the minimized functions of the flip-flop inputs using k-map. [3]
- C. Draw the logic diagram. [3]

3. Design a 3-bit Universal Shift Register with the functions given in the function table below. Here two control bits F and R determine the mode of operation. Use D Flip Flops for your design. [10]

F	R	Operation
0	0	Parallel Load
0	1	Shift Left
1	0	Toggle
1	1	Clear Register to 0

4. Okabe has 5 mobile phones, and each of his 5 friends can call him on one of these phones to leave a message. Since he can only check one message at a time, he needs to prioritize which message to check first if multiple phones ring simultaneously. His friends and their message codes are Kurisu (K-4), Mayuri (M-2), Luka (L-6), Faris (F-7), and Hashida (H-3). The first letter represents the friend (input), and the number represents the message code. For example, in "M-2", 'M' is the input, and "2" or "010" is the message code. The priority sequence Okabe uses to decide which message to check first is: M>K>H>L>F.

You have to answer the followings:

- A. Derive the truth table of the priority encoder including the valid bit. [3]  
 B. Derive the Optimal Boolean expressions for all the outputs. [3]  
 C. Draw the logic diagram using basic gates. [2]  
 D. If the inputs (M, K, H, L, F) are (0, 1, 1, 0, 1) whose message code will he read first? What is the message code?
5. A. Implement the following functions using a single decoder: [5]  
 $F1 = A'B'C'D + AB'CD + AB'C'D + A'BCD$   
 $F2 = (A + B + C + D)(A + B + C' + D)(A' + B' + C' + D)(A' + B' + C' + D')$   
 B. Implement the function  $F(A, B, C, D) = \prod_M(1,5,6,9,10,11,13)$  using a 4x1 MUX. [5]

Excitation Tables for D Flip-Flop

Q(t)	Q(t+1)	D	Operation
0	0	0	Reset
0	1	1	Set
1	0	0	Reset
1	1	1	Set