



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
MID Exam, Trimester: Spring 2025

Course Code: CSE 113/EEE 2113; Course Title: Electrical Circuits

Total Marks: 30; Duration: 1 hour 30 minutes

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

Question 1: Answer all the questions.

(8 Marks)

The current shown in **Figure 1** is flowing through a 10 ohm resistor; determine the following:

[4+4]
CO1

- i) **Sketch** the power vs time graph for this resistor.
- ii) **Sketch** the graph of charge flowing through this resistor vs time from 0s to 8s.

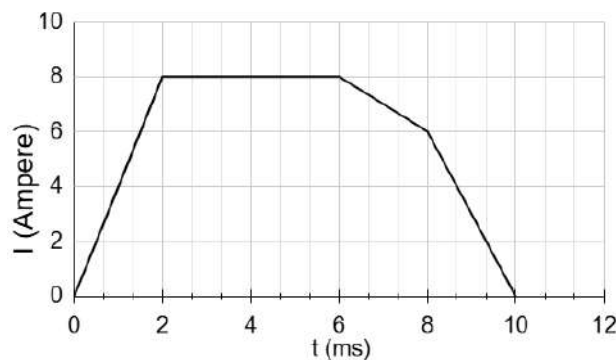


Figure 1

Question 2: Answer all the questions.

(6 Marks)

Observe the circuit in **Figure 2** and do the followings:

[2+2+2]
CO2

- i) Apply **KCL** at node **A** and develop an equation.
- ii) Apply **KVL** in **Loop 1** and **Loop 2** and develop two equations.
- iii) Determine I_y and the voltage of the R_4 resistor.

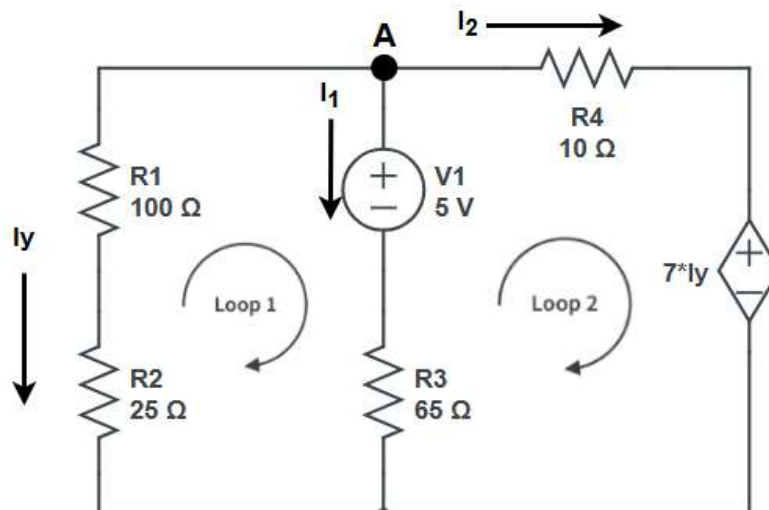


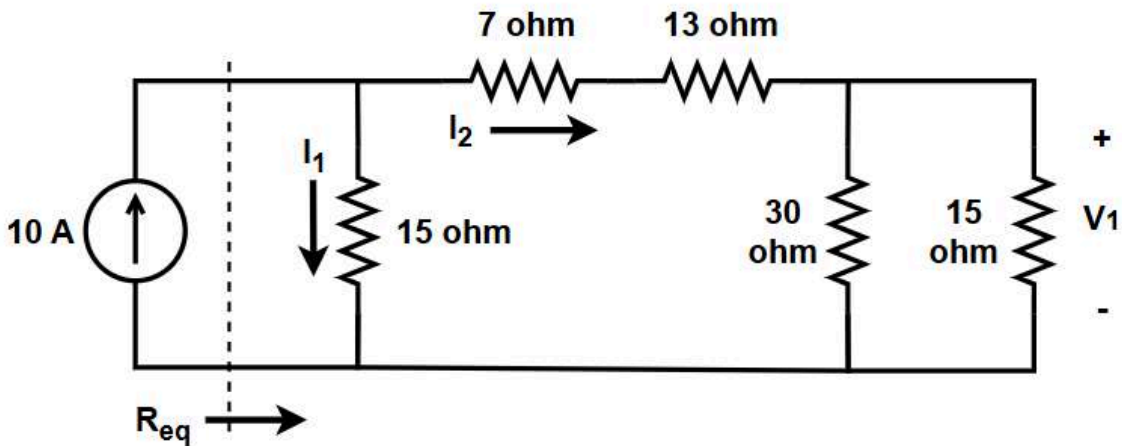
Figure 2

Question 3: Answer all the questions**(8 Marks)**

For the following circuit shown in **Figure 3**, **determine** the following:

- Find** the equivalent resistance, R_{eq} .
- Using only CDR, **find** the values of I_1 and I_2 .
- Find** the value of V_1 using VDR only.

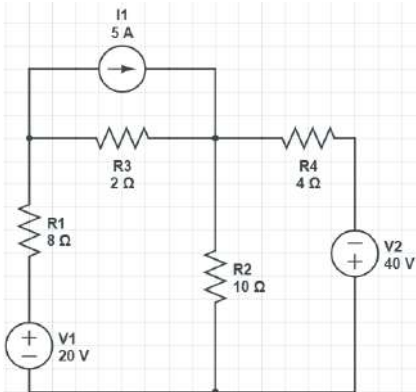
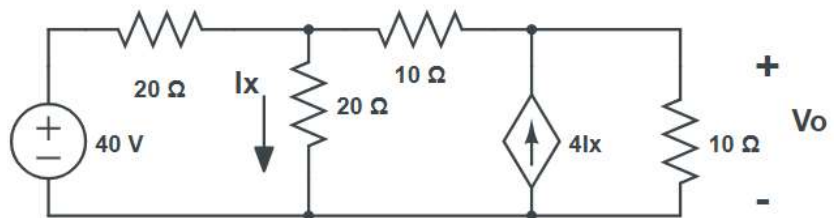
[2+4+2]
CO1

**Figure 3****Question 4: Answer all the questions.****(8 Marks)**

Answer the following questions for the circuit shown in **Figure 4(a)** and **4(b)**:

- Determine** the voltage across 10Ω using mesh analysis for the circuit shown in **Figure 4(a)**.
- Determine** the voltage V_o using nodal analysis for the circuit shown in **Figure 4(b)**.

[4+4]
CO2

**Figure 4(a)****Figure 4(b)**