



United International University (UIU)
Department of Computer Science and Engineering
CSE 1325: DIGITAL LOGIC DESIGN, Midterm Summer 2025

Total Marks: **30**, Duration: 1 hour 30 minutes

[Any examinee found adopting unfair means including copy from another examinee will be expelled from the trimester/program as per UIU disciplinary rules.]

Answer All Questions

1. A) Convert $(1432)_7$ and $(1180)_9$ to BCD (Binary Coded Decimal) format. Perform the BCD addition of the two numbers and show all necessary steps. [3]

- B) Find the values of the radix a and b from the following equations: [3]

$$\frac{(57)_a + (37)_b}{(112)_4} = \frac{49}{22}$$
$$\frac{(81)_b + (27)_a}{(221)_6} = \frac{56}{85}$$

2. A) Prove the identity of the following Boolean equation using algebraic manipulation: [3]

$$\bar{A}B(\bar{D} + \bar{C}D) + B(A + \bar{A}CD) = B$$

- B) Find the complement of the following function [3]

$$F(X, Y, Z) = (\bar{X} + Y + \bar{Z})(X + \bar{Y})(X + Z)$$

3. For the following Boolean function F, use K-Map And find the following:

$$F(a, b, c, d) = (\bar{a}bd + a\bar{c}\bar{d} + abd + ac\bar{d})$$

- A. Convert it to canonical form (SOM). [1]
B. Simplified sum-of-products (SOP) and [2]
C. Simplified product-of-sums (POS) form. [2]
D. Between minimized SOP and POS, which form will you choose to implement the function and why? [1]

4. Consider the following Boolean function:

$$F(A, B, C, D) = \sum_m(0, 1, 4, 6, 7, 9, 11, 13, 14) + \sum_d(3, 5, 8)$$

- A. Find all the Prime Implicants and [2]
B. determine which of the Prime Implicants are Essential. [2]
C. Find the optimal solution using selection rule. [2]

5. Consider a smart smoothie maker that checks the taste of a smoothie depending on the fruits added. The system checks the presence of four types of fruits: mangoes (M), watermelons (W), lemons (L), and passion fruits (P). Mango and watermelon are sweet fruits, while lemon and passion fruit are sour. If the value of a variable is **1** that means the fruit is present in the smoothie and **0** means the fruit is absent from the smoothie. The smoothie is considered **sweet (output 1)** if there are more sweet fruits (mangoes and watermelons) than sour fruits (lemons and passion fruits). It is considered **sour (output 0)** if the number of sour fruits is greater than or equal to the number of sweet fruits. The output is **don't care (X)** if there are no fruits present at all.

Design a Boolean function **F** that can be used to make a circuit to check these conditions in the smoothie maker.

You have to

- A. Draw the truth table. [2]
- B. Find the simplified expression for the output bit in Sum-of-Product (SOP) form using K-map. [3]
- C. Draw the circuit diagram using basic gates. [1]

Example:

- Input 1000 → Output = 1 (Mango only → sweet majority)
- Input 0011 → Output = 0 (Lemon + Passion fruit → sour majority)
- Input 0110 → Output = 0 (Watermelon + Lemon → equal number of sweet and sour fruits)
- Input 0000 → Output = X (No fruits → Don't care)