

1. Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.
2. You must write your serial Number on the top of your Exam's Answer Sheet.

Question 1: Answer all the questions.

(15 Marks)

Rashed and Tanvir built a linear DC circuit with a variable load resistor connected across terminals a–b. Rashed claims that connecting a $4\ \Omega$ resistor across terminals a–b will ensure maximum power transfer. Tanvir disagrees, stating that maximum power transfer occurs when a $3.5\ \Omega$ resistor is connected across terminals a–b. Now, answer the following questions: [8+2+2+2+1]
CO3

- i) **Determine** the Thevenin equivalent circuit seen from terminals a–b.
- ii) **Calculate** the current flowing through the load resistance when the load is $4\ \Omega$, and then when the load is $3.5\ \Omega$.
- iii) **Calculate** the power delivered to the load when following Rashed's advice, and then calculate the power delivered to the load when following Tanvir's advice.
- iv) **Explain** when the maximum power is delivered to the load and whose claim (Rashed's or Tanvir's) is correct.
- v) If you want to connect a bulb between a-b for maximum power, **what** could be the rating of this bulb? Rating of a bulb means the typical operating voltage of a bulb and its corresponding power.

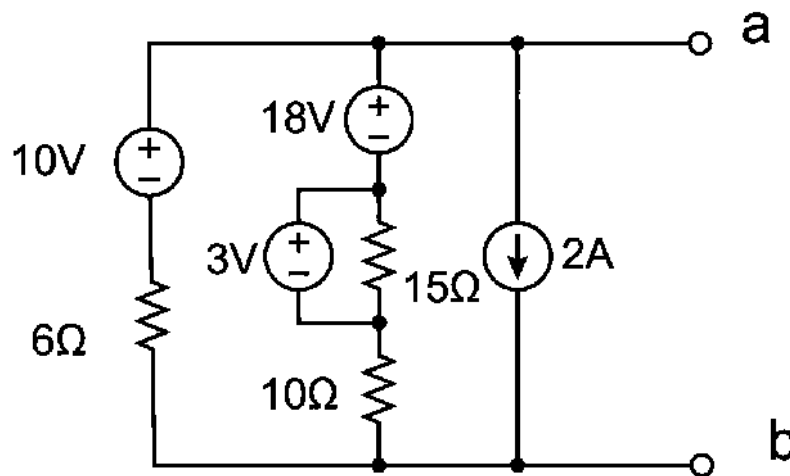
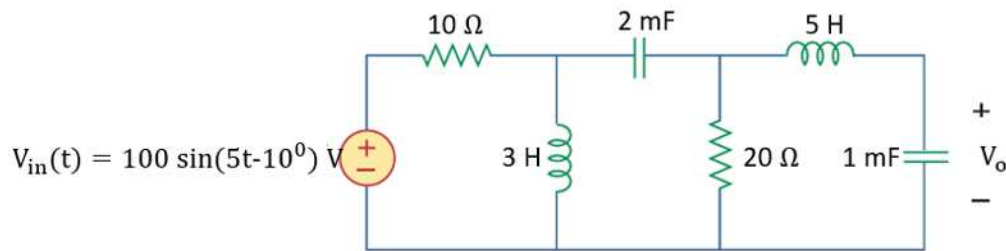


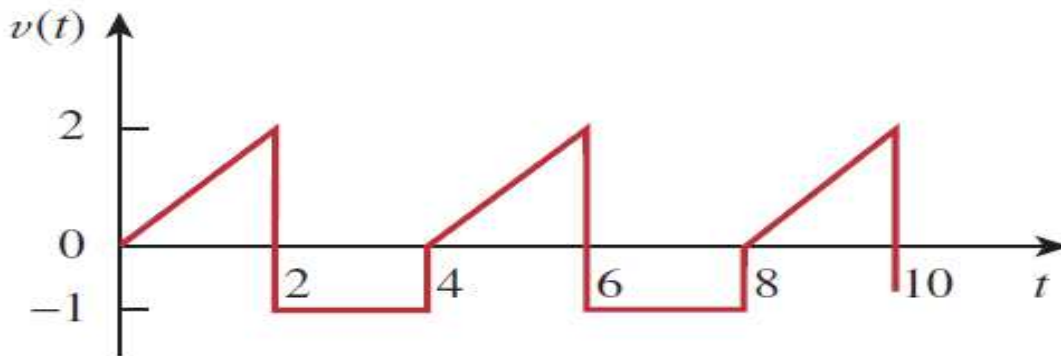
Figure 1

Question 2: Answer all the questions.**(15 Marks)**For the circuit shown in **Figure 2**, answer the following questions:[5+4+
4+2]
CO4**Figure 2**

- Redraw** the circuit in the phasor domain and **determine** the equivalent impedance as seen by the sinusoidal voltage source.
- Determine** $V_o(t)$ using CDR or VDR.
- Determine** the phase angle difference between the input, $V_{in}(t)$, and output voltage, $V_o(t)$, and find by how much the output voltage is lagging.
- Calculate** the average real power absorbed by the 20Ω resistor.

Question 3: Answer all the questions.**(10 Marks)**A 10Ω resistor receives a **periodic voltage $v(t)$** across it. The waveform is shown below.[4+4+
2]
CO4

- Derive** the mathematical expression of $v(t)$.
- Determine** the rms value of $v(t)$.
- Determine** the power absorbed by the resistor.

**Figure 3**