

Question 1: Answer all the questions.

(12 Marks)

A linear source network (Figure 1) is accessible through its output terminals A-B. The network contains an unknown internal resistance (R). An experimental measurement obtained by connecting a load across the terminals showed $V_{AB} = 160$ V while $I_a = 3$ A flowed into the load.

[6+4+2]
CO3

- Determine** the Thevenin equivalent voltage and resistance of the source network. (Note: Use the general approach as well as the data provided across the variable load while determining the Thevenin voltage and current)
- Using the Thevenin resistance calculated above, **find** the value of the internal resistance (R).
- Calculate** the maximum power that can be extracted from the network and **specify** the corresponding load resistance.

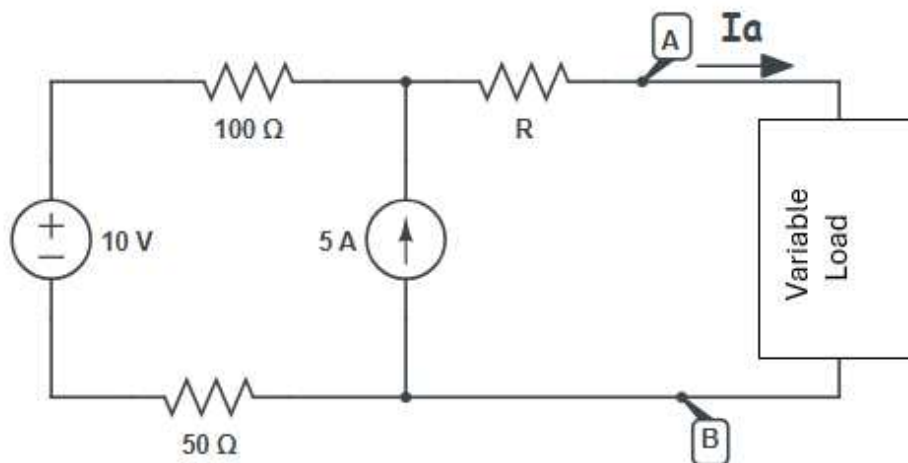


Figure 1

Question 2: Answer all the questions.

(8 Marks)

- For **Figure 2**, find the current, i , using the superposition theorem.
- Validate** the superposition theorem by finding the value of i without using superposition (you can use other methods except superposition theorem).

[4+4]
CO3

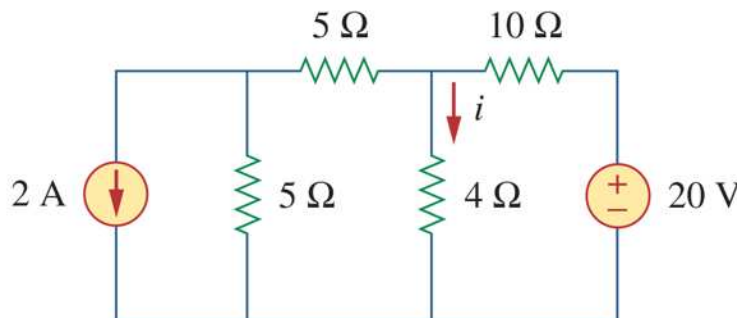


Figure 2

Question 3: Answer all the questions

(12 Marks)

For **Figure 3**, answer the following questions:

- I. **Determine** the value of Z_x and **the total impedance** of this circuit if $V_{L1} = 2 \angle -35^\circ$ and $I_z = 0.148 \angle 20^\circ$.
- II. **What** electric components (Resistors/Capacitors/Inductors) are used in Z_x , and **determine** their values.
- III. **Determine** the source voltage's expression $V_1(t)$.
- IV. **Explain** if this AC circuit's behaviour can be changed from inductive to a capacitive nature by changing the source's frequency. (**Note:** An AC circuit shows inductive behavior when its total impedance has positive reactance, and capacitive behavior when its total impedance has negative reactance.)

[6+2+2
+2]
CO4

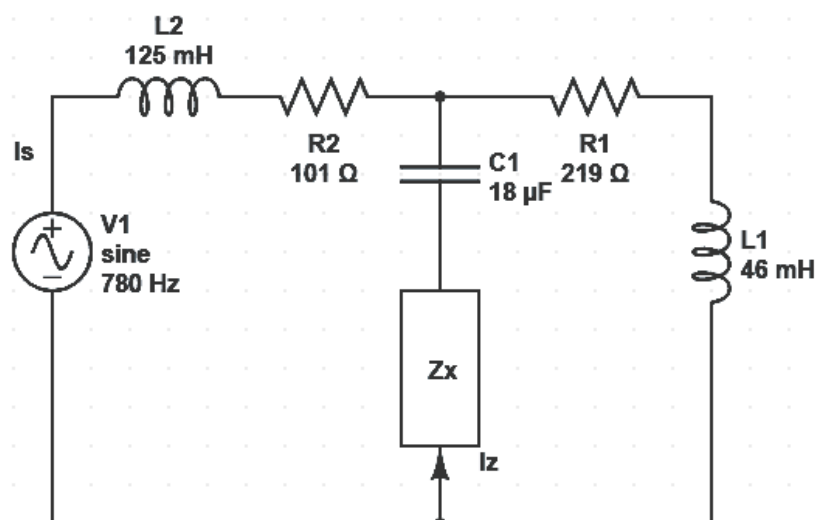


Figure 3

Question 4: Answer all the questions.

(8 Marks)

A 10Ω resistor receives a periodic voltage $v(t)$ across it. The waveform is shown below (**Figure 4**). Answer the following questions:

[2+6]
CO4

- I. **Derive** the mathematical expression of $v(t)$.
- II. **Determine** the power absorbed by the resistor.

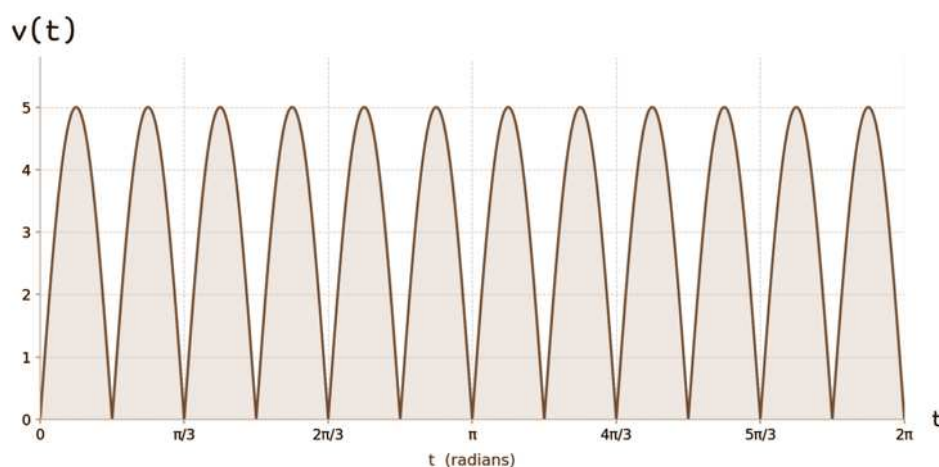


Figure 4