



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
Final-Term Exam: Trimester: Fall 2025

Course Code: EEE 2123; Course Title: Electronics
Total Marks: 40; Duration: 2hr

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

There are six (6) questions in this paper. Answer all of them.

1. Consider an NMOS transistor fabricated in a $0.18\text{-}\mu\text{m}$ process with $L = 0.18\text{ }\mu\text{m}$ and $W = 2\text{ }\mu\text{m}$. The process technology is specified to have $C_{ox} = 8.6\text{ fF}/\mu\text{m}^2$, $\mu_n = 450\text{ cm}^2/\text{V.s}$ and $V_{tn} = 0.5\text{ V}$.
 - (a) Find V_{GS} and V_{DS} that result in the MOSFET operating at the edge of saturation with $I_D = 100\text{ }\mu\text{A}$. [4]
 - (b) If V_{GS} is kept constant, find V_{DS} that results in $I_D = 50\text{ }\mu\text{A}$. (Triode region) [3]
2. From the circuit of Fig 2,
 - a. Analyze the circuit (Fig 2) to determine I_D , I_S , V_D , V_S , V_G , and I_G . Let $V_t = 1.2\text{ V}$, $K'_n(W/L) = 1\text{ mA}/\text{V}^2$. Assume $\lambda = 0$. [5]
 - b. What is the minimum value of R_D required for the MOSFET to operate in the linear region? [5]

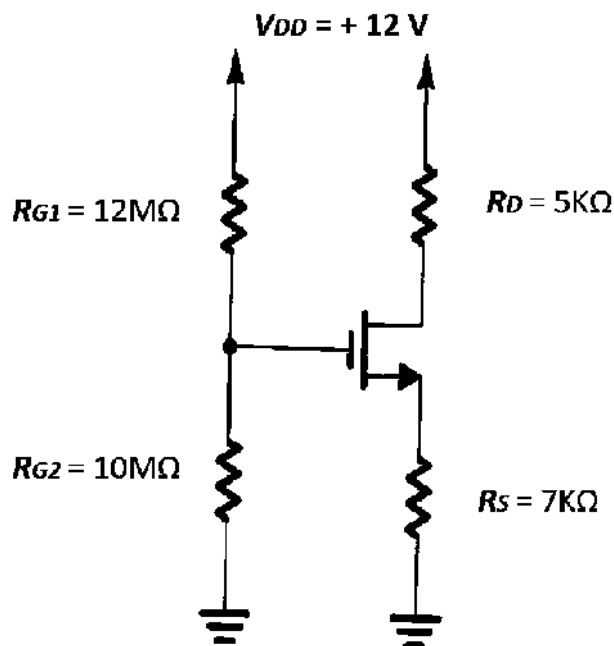


Fig 2: Figure for question 2

3. From the circuit of Fig 3, Find all node voltages and branch currents in the following circuit, $\beta = 100$ [6]

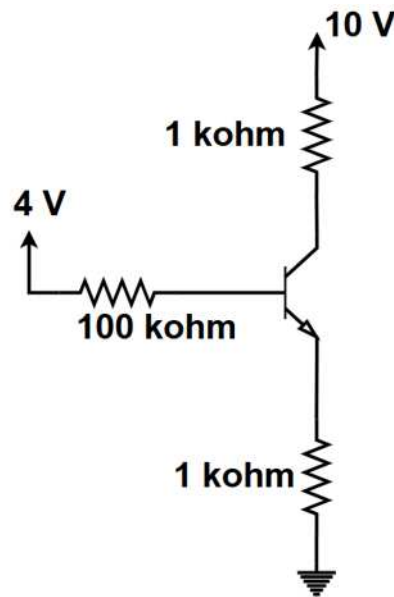


Fig 3: Figure for question 3

4. From the circuit of Fig 4, The BJT in Fig 4 is deep in saturation. Find the values of α and β of the BJT. [5]

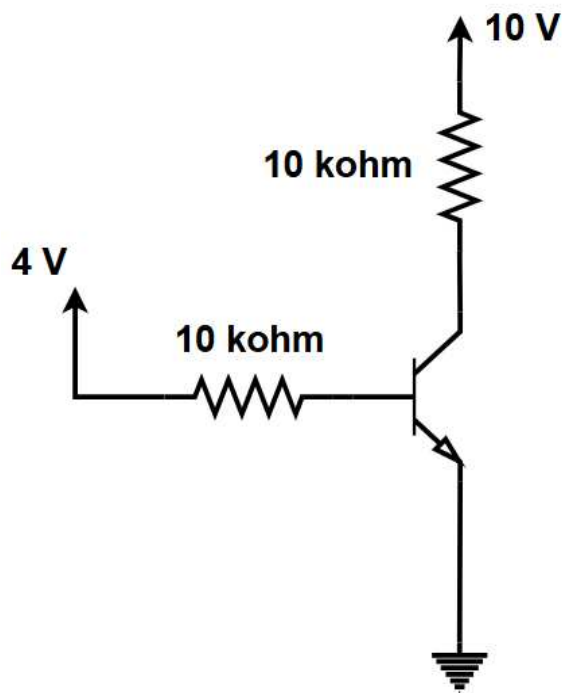


Fig 4: Figure for question 4

5. (a) From the circuit of Fig 5, The **PMOS** network of a random digital system is given below. Draw the **NMOS** network and determine the output logic. [3]

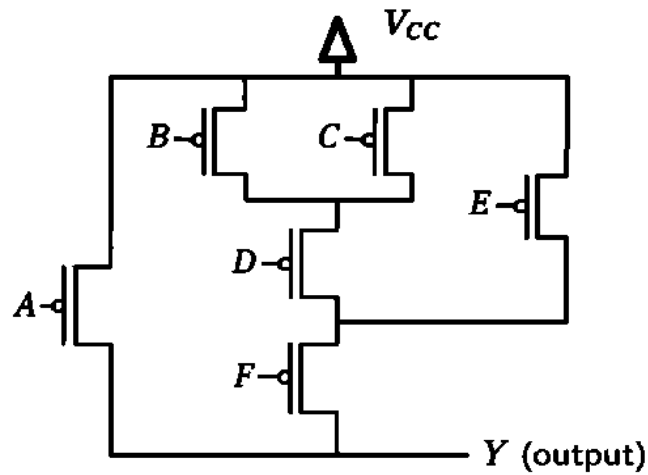


Fig 5: Figure for question 5 (a)

- (b) Implement the following logic function using CMOS: [3]

$$Y = ((a + b) \bar{c} + de) \bar{f}$$

6. Implement the following equation using Op-Amps: [6]

$$V_o = 2V_1 - 3V_2$$