



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
Final-Term Exam: Trimester: Spring 2026

Course Code: EEE 2123; Course Title: Electronics
Total Marks: 40; Duration: 2 Hours

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

There are six (6) questions in this paper. Answer all of them.

1. In the circuit of **Fig 1**, assume a constant $200 \mu\text{A}$ current flows through R . If both the MOSFETs have $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $W/L = 20$ then determine the values of V_1 , V_2 and V_3 .
(Hint: $200 \mu\text{A}$ Current will be equally divided between the 2 mosfets) [7]

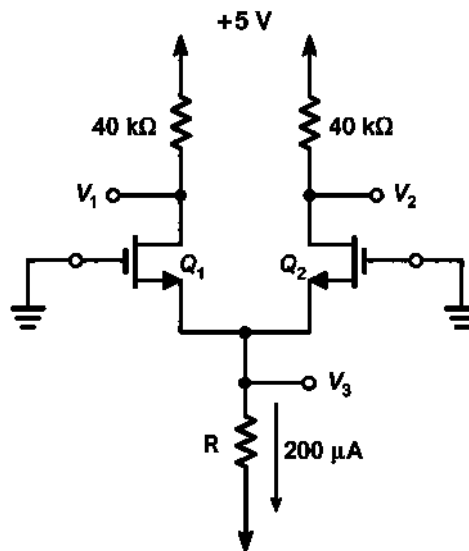


Fig 1: Figure for question 1

2. Analyze the circuit in **Fig 2** to determine voltages at all nodes and the currents through all branches. Let, $V_{tn} = 1\text{V}$, $k_n' W/L = 1 \text{ mA}/\text{V}^2$ [8]

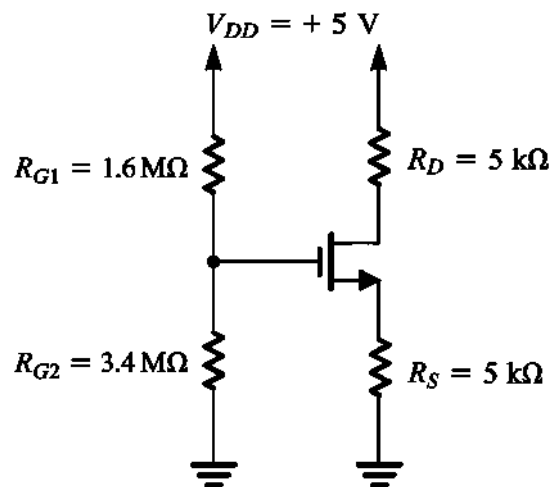


Fig 2: Figure for question 2

3. From the circuit of **Fig 3**, Find all node voltages and branch currents in the following circuit, $\beta = 120$ [6]

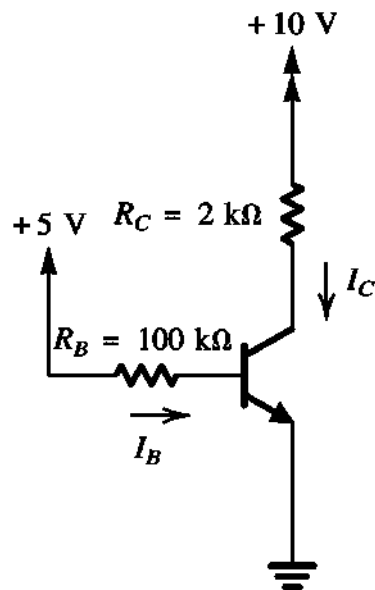


Fig 3: Figure for question 3

4. The BJT in **Fig 4** is operating at the edge of saturation ($V_{CE} = 0.3\text{ V}$, $\beta = 100$) . If $R_{B1} = 70\text{ k}\Omega$, determine the value of R_{B2} , all node voltages and branch currents. [7]

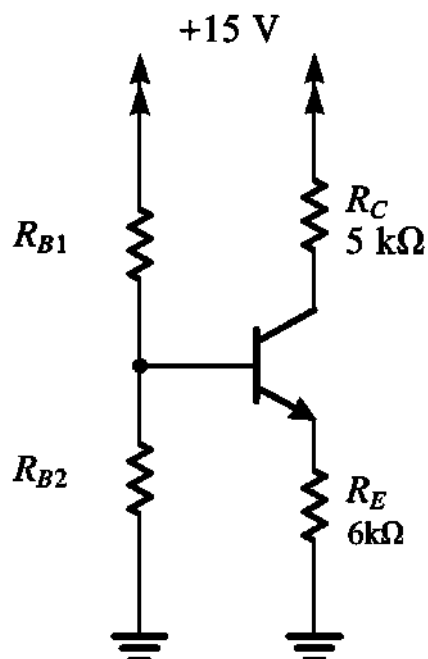


Fig 4: Figure for question 4

5. a) A battery-powered wearable device uses CMOS technology for its digital circuits. Explain why CMOS is a suitable choice for this application in terms of power efficiency. [2]

b) Implement the following boolean expression using CMOS technology. You cannot use more than 4 NMOS and 4 PMOS. [4]

$$F = \overline{(A + B)(A + C\overline{B} + CB\overline{D} + CBD)}$$

6. a) In the Op-Amp circuit of **Fig 6**, V_1 and V_2 are inputs and V_o is the output. The circuit has the output expression given below. Find the values of R and C in the circuit. [3]

$$V_o = 2\frac{dV_2}{dt} - 6V_1$$

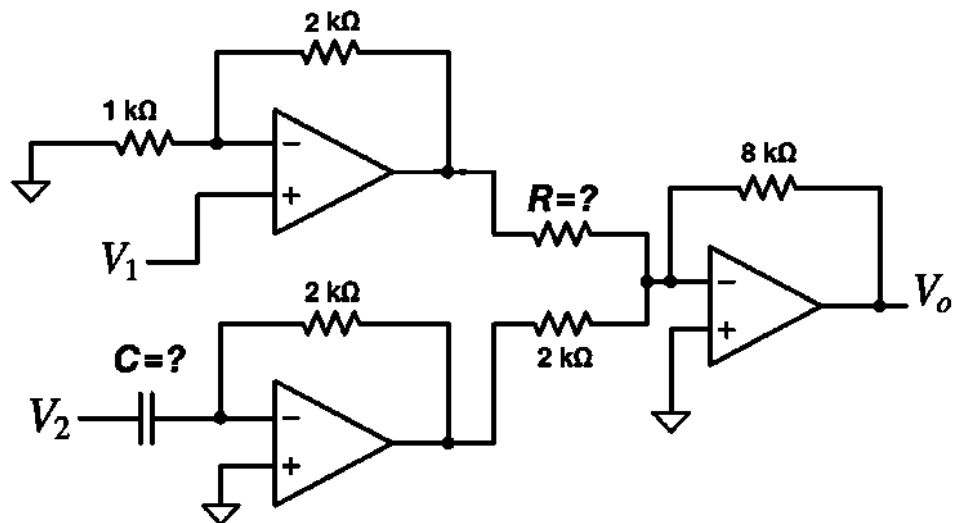


Fig 6: Figure for question 6(a).

- b) Implement the following expression using op-amps. [3]

$$V_o = 4V_1 + 7V_2$$